

CS 223 Digital Systems
Fall 2011
Verilog
Computer Engineering Dept
Bilkent University

Behavioral Modelling

- Behavioral Models represent functionality of the digital hardware.
- It describes how the circuit will operate without specifying hardware.
- There are two important keywords for behavioral description.
- **initial** Specifies a single-pass behavior.
- **always** Specifies cyclic behavior.

Behavioral Modelling

- **initial** keyword is followed by a single statement or a **begin.. end** block
- The statement following **initial** is executed once at $t=0$ and it expires.
- **always** keyword is followed by a single statement or a **begin.. end** block
- The statement following **always** is executed repeatedly until simulation is stopped.

Use of initial and always.

initial

begin //defines a clock with 20 unit clock period.

clock=1'b0;

repeat(30) // clock will operate for 300 units.

#10 clock=~clock;

end

Use of initial and always.

initial

begin

```
clock=1'b0;
```

end

initial #300 \$finish; // clock will operate for 300 units.

always #10 clock=~clock; //defines a clock with 20 unit clock period.

System task **\$finish** causes simulation to terminate.

always and event control @

```

always @(event control expression)
begin
    .....
end

```

- @ is called event control operator.
- **always** @(event) waits until the event occurs.
- When event takes place **begin.. end** block will be executed.
- Example: wait for positive edge of clock
always @(posedge clock)
always @(posedge clock or negedge reset)

Blocking and Nonblocking Assignments

- Blocking assignments use (=) as assignment operator

Blocking and Nonblocking Assignments

- Blocking assignments use (=) as assignment operator
- Blocking assignments are executed *sequentially*.

Blocking and Nonblocking Assignments

- Blocking assignments use (=) as assignment operator
- Blocking assignments are executed *sequentially*.
- Nonblocking assignments use (<=) as assignment operator

Blocking and Nonblocking Assignments

- Blocking assignments use (=) as assignment operator
- Blocking assignments are executed *sequentially*.
- Nonblocking assignments use (<=) as assignment operator
- Nonblocking assignments are executed *concurrently*.

Blocking and Nonblocking Assignments

- If $A=3$ and $B=5$

Blocking and Nonblocking Assignments

- If $A=3$ and $B=5$
- $B=A$

Blocking and Nonblocking Assignments

- If $A=3$ and $B=5$
- $B=A$
- $C=B+2$ will set $B=3$ and $C=5$

Blocking and Nonblocking Assignments

- If $A=3$ and $B=5$
- $B=A$
- $C=B+2$ will set $B=3$ and $C=5$
- $B<=A$

Blocking and Nonblocking Assignments

- If $A=3$ and $B=5$
- $B=A$
- $C=B+2$ will set $B=3$ and $C=5$
- $B<=A$
- $C<=B+2$

Blocking and Nonblocking Assignments

- If $A=3$ and $B=5$
- $B=A$
- $C=B+2$ will set $B=3$ and $C=5$
- $B<=A$
- $C<=B+2$
- result $B=3$ and $C=7$

D-flip-flop Description

```
module D_flip_flop (Q, D, CLK);  
output Q;  
input D, CLK;  
reg Q;  
always @ (posedge CLK)  
Q <= D;  
endmodule
```

D flip-flop Description

```
module D_flip_flop_b (Q, Q_b, D, CLK);  
output Q, Q_b;  
input D, CLK;  
reg Q;  
assign Q_b = ~Q;  
always @ (posedge CLK)  
Q <= D;  
endmodule
```

D flip-flop with active-low asynchronous reset

```
// Description of D flip-flop
// with active-low asynchronous reset
module D_flip_flop_AR (Q, D, CLK, RST);
output Q;
input D, CLK, RST;
reg Q;
always @ (posedge CLK, negedge RST)
if (RST == 0) Q <= 1'b0;
else Q <= D;
endmodule
```

D flip-flop with active-low asynchronous reset

```
module D_flip_flop_AR_b (Q, Q_b, D, CLK, RST);  
output Q, Q_b;  
input D, CLK, RST;  
reg Q;  
assign Q_b = ~Q;  
always @ (posedge CLK, negedge RST)  
if (RST == 0) Q <= 1'b0;  
else Q <= D;  
endmodule
```

D-flip-flop test

```
module t_D_flip_flops;  
wire Q, Q_AR;  
reg D, CLK, RST;  
D_flip_flop M0 (Q, D, CLK);  
D_flip_flop_AR M1 (Q_AR, D, CLK, RST);  
initial #100 $finish;  
initial begin CLK = 0; forever #5 CLK = ~CLK; end
```


D-flip-flop test continued

```
initial fork
D = 1;
RST = 1;
#20 D = 0; #40 D = 1;
#50 D = 0; #60 D = 1;
#70 D = 0; #90 D = 1;
#42 RST = 0; #72 RST = 1;
join
endmodule
```

fork and join

- **forkjoin** pair specifies that the statements inside fork and join are to be done in parallel.
- The statement delays are with respect to time 0 and each statement is executed independent of others.
- The common variables are updated by each statement. One should be careful so that race conditions should not take place.

Example State Diagram

 

Moore FSM

```
module Moore_Model_1( output [1: 0] y_out,  
input x_in, clock, reset );  
reg [1: 0] state;  
parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;  
always @ (posedge clock, negedge reset)  
if (reset == 0) state <= S0; // Initialize to state S0  
else case (state)  
S0: if (~x_in) state <= S1; else state <= S0;  
S1: if (x_in) state <= S2; else state <= S3;  
S2: if (~x_in) state <= S3; else state <= S2;  
S3: if (~x_in) state <= S0; else state <= S3;  
endcase  
assign y_out = state; // Output of flip-flops  
endmodule
```



Moore FSM test)

```
module t_Moore_Model_1;
wire [1: 0] t_y_out;
reg t_x_in, t_clock, t_reset;
Moore_Model_1 M0 (t_y_out, t_x_in, t_clock, t_reset);
initial #200 $finish;
initial begin t_clock = 0; forever #5 t_clock = ~t_clock; end
initial fork
t_reset = 0;
#2 t_reset = 1;
#87 t_reset = 0;
#89 t_reset = 1;
#10 t_x_in = 1;
#30 t_x_in = 0;
#40 t_x_in = 1;
```

Moore FSM test

```
#50 t_x_in = 0;
#52 t_x_in = 1;
#54 t_x_in = 0;
#70 t_x_in = 1;
#80 t_x_in = 1;
#70 t_x_in = 0;
#90 t_x_in = 1;
#100 t_x_in = 0;
#120 t_x_in = 1;
#160 t_x_in = 0;
#170 t_x_in = 1;
join
endmodule
```

State Diagram Fig 5-20

 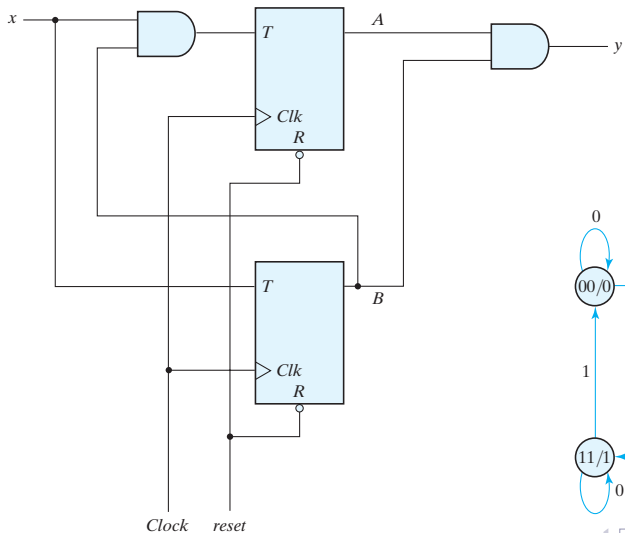

State Diagram Fig 5-20

```
module Moore_Model_STR_Fig_5_20 (  
output y_out, A, B,  
input x_in, clock, reset  
);  
wire TA, TB;  
// Flip-flop input equations  
assign TA = x_in & B;  
assign TB = x_in;  
//output equation  
assign y_out = A & B;  
// Instantiate Toggle flip-flops  
Toggle_flip_flop_3 M_A (A, TA, clock, reset);  
Toggle_flip_flop_3 M_B (B, TB, clock, reset);  
endmodule
```